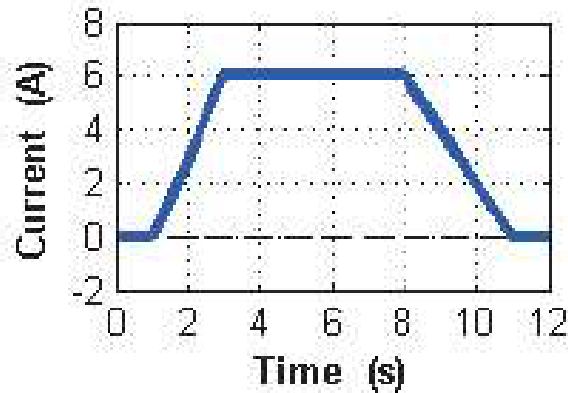


BLM1612 - Circuit Theory

Examples

Example 01

- Given the following current graph through an element, what is the net charge that passes through the element between $t = 4$ and $t = 8$ seconds?




$$q = \int_{t_1}^{t_2} i dt = \int_4^8 6 dt = 6t \Big|_4^8 = 6(8 - 4) = 24 \text{ C}$$

– or for constant current

$$q = i \times \Delta t = 6(8 - 4) = 24 \text{ C}$$

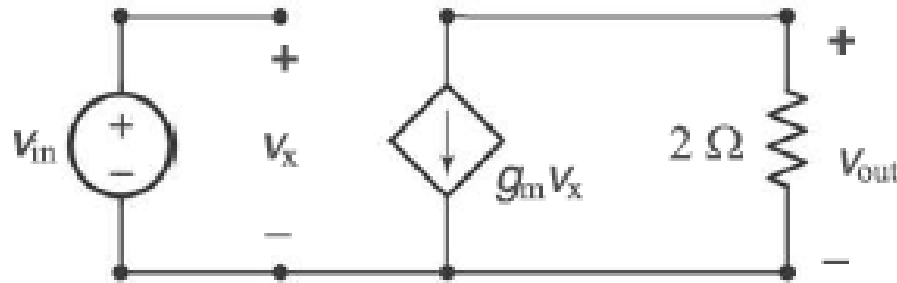Example 02

- In the circuit below, $v_{in}=3\sin(\omega t)$ mV and $g_m=10$ A/V. Determine v_{out} .




$$v_{out} = -g_m v_x \times R$$

$$v_{out} = -10 \times 3\sin(\omega t) \times 2$$

$$v_{out} = -60\sin(\omega t) \text{ mV}$$

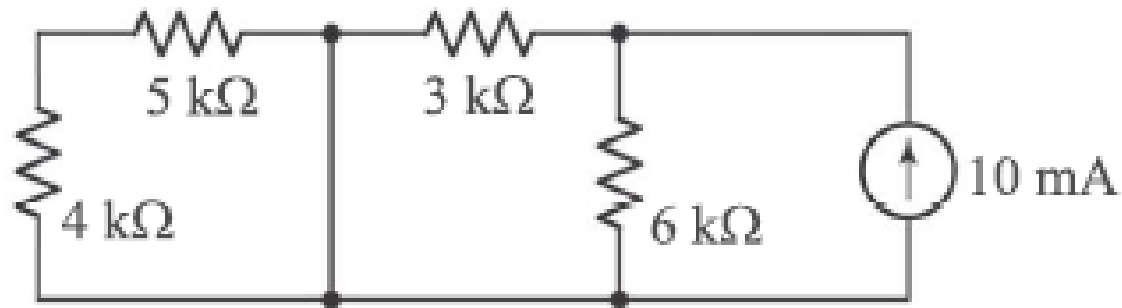Example 03


- In the circuit below, determine the power absorbed by the 5 k Ω resistor.




- Short circuit across 4 k Ω and 5 k Ω resistors.
 - No current through 5 k Ω resistor.
- Therefore

$$P_{\text{abs}} = 0 \text{ W}$$

Example 04...

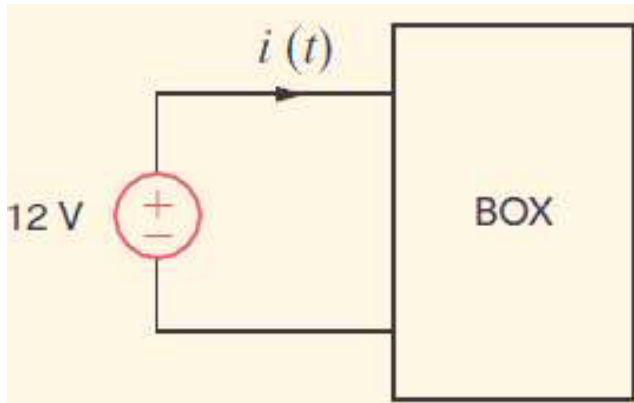

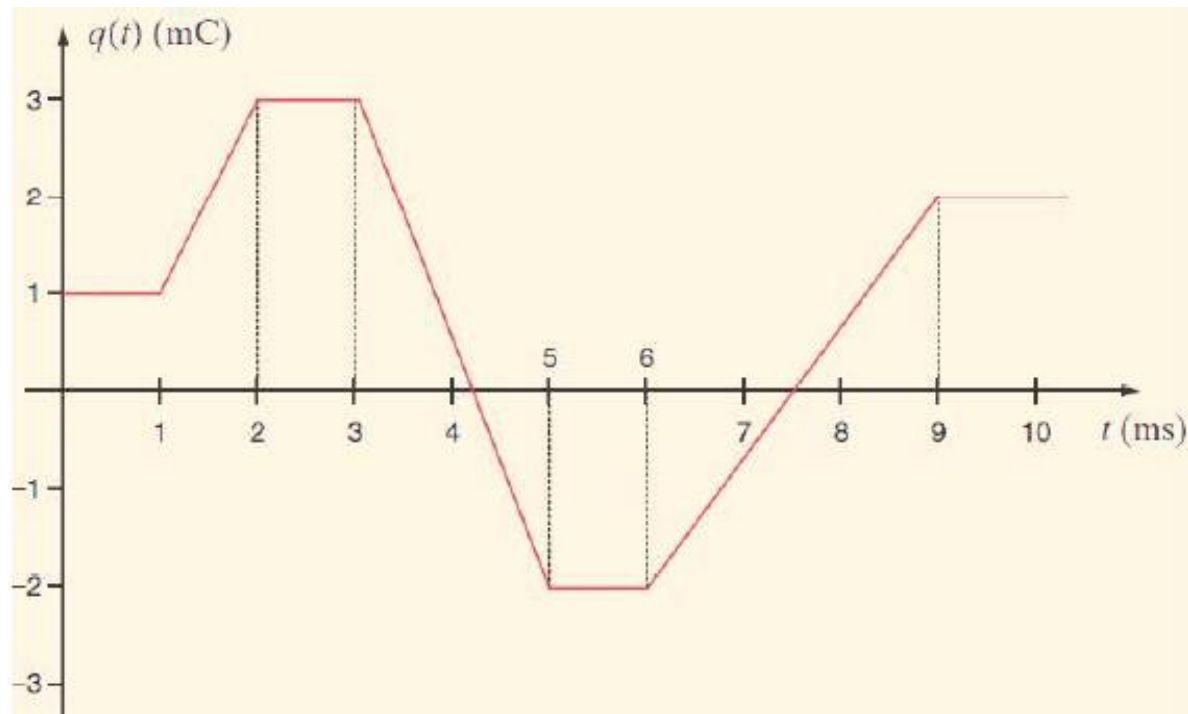- The charge that enters the BOX is given below. Calculate and sketch the current flowing into and the power absorbed by the BOX between 0 and 10 ms.



$$i(t) = \frac{dq(t)}{dt}$$

...Example 04...

Recall that current is related to charge by $i(t) = \frac{dq(t)}{dt}$. The current is equal to the slope of the charge waveform.

$$i(t) = 0 \qquad 0 \leq t \leq 1 \text{ ms}$$

$$i(t) = \frac{3 \times 10^{-3} - 1 \times 10^{-3}}{2 \times 10^{-3} - 1 \times 10^{-3}} = 2 \text{ A} \qquad 1 \leq t \leq 2 \text{ ms}$$

$$i(t) = 0 \qquad 2 \leq t \leq 3 \text{ ms}$$


$$i(t) = \frac{-2 \times 10^{-3} - 3 \times 10^{-3}}{5 \times 10^{-3} - 3 \times 10^{-3}} = -2.5 \text{ A} \qquad 3 \leq t \leq 5 \text{ ms}$$

$$i(t) = 0 \qquad 5 \leq t \leq 6 \text{ ms}$$

$$i(t) = \frac{2 \times 10^{-3} - (-2 \times 10^{-3})}{9 \times 10^{-3} - 6 \times 10^{-3}} = 1.33 \text{ A} \qquad 6 \leq t \leq 9 \text{ ms}$$

$$i(t) = 0 \qquad t \geq 9 \text{ ms}$$

...Example 04...

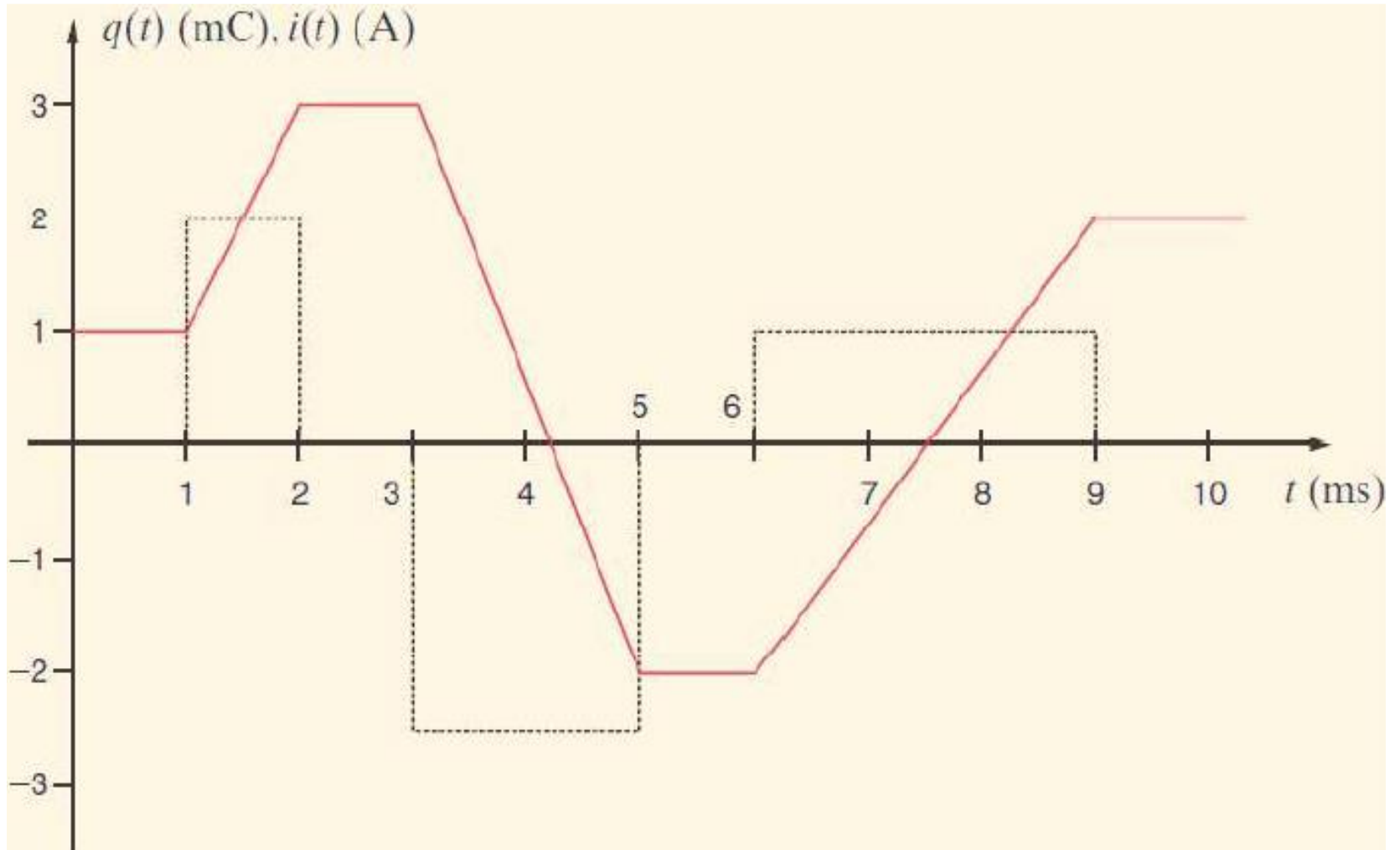

...Example 04

The power absorbed by the BOX is $12 \cdot i(t)$.

$$p(t) = 12 \cdot 0 = 0 \quad 0 \leq t \leq 1 \text{ ms}$$

$$p(t) = 12 \cdot 2 = 24 \text{ W} \quad 1 \leq t \leq 2 \text{ ms}$$

$$p(t) = 12 \cdot 0 = 0 \quad 2 \leq t \leq 3 \text{ ms}$$

$$p(t) = 12 \cdot (-2.5) = -30 \text{ W} \quad 3 \leq t \leq 5 \text{ ms}$$

$$p(t) = 12 \cdot 0 = 0 \quad 5 \leq t \leq 6 \text{ ms}$$

$$p(t) = 12 \cdot 1.33 = 16 \text{ W} \quad 6 \leq t \leq 9 \text{ ms}$$

$$p(t) = 12 \cdot 0 = 0 \quad t \geq 9 \text{ ms}$$

