

A one-quadrant dc chopper with 200V supply voltage and 5 kHz switching frequency controls the power of 10Ω heater. For $\lambda = 1/4$ by ignoring circuit losses

- Calculate the period and t_{on}
- Calculate the load current while the transistor is on
- Find the average and rms value of the transistor
- Find the input power of the dc chopper

$$a) T_s = \frac{1}{f_s} = \frac{1}{5 \cdot 10^3} = 200 \mu s$$

$$D = \frac{T_{on}}{T_s} = \frac{1}{4} \Rightarrow t_{on} = 50 \mu s.$$

$$b) I_o = \frac{V_s}{R \rightarrow \text{load}} = \frac{200}{10} = 20 A.$$

$$I_o = I_{Load}$$

$$c) I_{TAV} = D \cdot I_o = \frac{1}{4} \cdot 20 = 5 A.$$

$$I_{TRMS} = \sqrt{D} \cdot I_o = \sqrt{\frac{1}{4}} \cdot 20 = 10 A.$$

$$d) P_i = V_s \cdot I_{TAV} = 200 \cdot 5 = 1 \text{ kW}.$$

Example

A dc motor with 250V input voltage is controlled via a dc chopper with 1kHz operational frequency.

The data for the motor is given as following for nominal operation: $P = 1750 \text{ W}$, $n = 1000 \text{ rpm}$

$U = 200 \text{ V}$, $I_a = 10 \text{ A}$, $R_a = 2 \text{ } \Omega$, $P_{\text{loss}} = 0$, I_{field} is constant (Torque, constant).

a) If $D = \frac{3}{5}$ at single quadrant dc chopper, For nominal torque value, Find out, E_a Back e.m.f, number of revolution (n), Motor input power, torque and efficiency of motor.

Solution

$$E_a + R_a \cdot I_a = U \text{ (motor voltage)}$$

$$U_0 = D \cdot 250 \rightarrow \text{input voltage of dc chopper}$$

$$U_0 = \frac{3}{5} \cdot 250 = 150 \text{ V. } \left[\begin{array}{l} \text{output voltage dc chopper and} \\ \text{input voltage of dc motor} \end{array} \right]$$

$$E_a = U_0 - I_a \cdot R_a = 150 - 2 \cdot 10 = 130 \text{ V.}$$

$$E_a = k \cdot \Phi \cdot n \rightarrow (I_{\text{field}} = \text{constant, means } \Phi \text{ constant})$$

$$E_a = C \cdot n$$

$$\frac{E_{a_n}}{E_a} = \frac{n_n}{n} \Rightarrow E_{a_n} = 200 - 2 \cdot 10 = 180 \text{ V.}$$

$n = 1000$

$$\frac{180}{130} = \frac{1000}{n} \Rightarrow n = 722.2 \text{ rpm.}$$

$$P_i = U_0 \cdot I_a = 150 \cdot 10 = 1500 \text{ W.}$$

$$P_o = P_{\text{mech}} \approx E_a \cdot I_a = 130 \cdot 10 = 1300 \text{ W}$$

$$\eta = \% \frac{P_{in}}{P_o} = \frac{1300}{1500} = \% 86.$$

$$P_o = P_{mech} = T \cdot \omega = T \cdot \frac{2 \cdot \pi \cdot n}{60}$$

$$T = \frac{1300}{2 \cdot \pi \cdot \frac{722.2}{60}} = 17.19 \text{ Nm.}$$

b) Let's assume that the dc motor is controlled by a two quadrant dc chopper and it rotates at 500 rpm. Find out the D, Ton and T values for braking with nominal torque value.

$$n = 500 \text{ rpm.}$$

$$\frac{E_a n}{E_a} = \frac{n n}{500} = \frac{180}{E_a} = \frac{1000}{500} \Rightarrow E_a = 90 \text{ V}$$

$$\text{For braking } E > U \text{ means } E_a = U + R_a \cdot I_a$$

$$E_a = 90 = U + 2 \cdot 10 \Rightarrow U = 70 \text{ V.}$$

70V is the output voltage of the dc chopper

We know the input voltage of the dc chopper

$$250 = D \cdot 70 \Rightarrow D = 0.36$$

$$T = \frac{1}{f} = \frac{1}{1000} = 1 \text{ ms}$$

$$T_{on} = D \cdot T = 0.36 \text{ ms}$$

$$T = T_{on} + T_{off} \Rightarrow T_{off} = 0.64 \text{ ms.}$$

A two quadrant dc/dc converter (dc chopper) with 100 V. input voltage and 20 kHz operational frequency supplies to a dc motor with 10A nominal current value. By assuming the output current is constant;

- a) If $D = 7/10$, find out the voltage across the load, the power of dc motor, diode and transistor currents.
- b) If $D = 2/10$, what about the direction of power flow, please comment it

$$a) \quad U_o = \frac{1}{T} \left[\int_0^{T_{on}} U_d \cdot dt + \int_{T_{on}}^T -U_d \cdot dt \right]$$

$$D = \frac{T_{on}}{T}$$


$$U_o = \frac{1}{T} \cdot (2 \cdot T_{on} - T) \cdot U_d$$

$$U_o = (2 \cdot D - 1) \cdot U_d$$

$$U_o = (2 \cdot \frac{7}{10} - 1) \cdot 100 = 40 \text{ V.}$$

$$I_T = \frac{7}{10} \cdot I_o = 7 \text{ A.}$$

$$I_D = 10 - 7 = 3 \text{ A.}$$

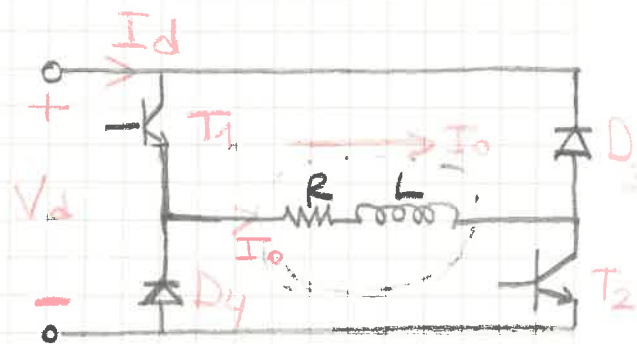

$$I_o = I_T + I_D$$

$$I_d = I_T - I_D$$

$$I_T = D \cdot I_o$$

$$P_o = U_o \cdot I_o = 10 \cdot 40 = 400 \text{ W}$$

$$b) \quad U_o = (2 \cdot \frac{2}{10} - 1) \cdot 100 = -60 \text{ V.}$$

Negative operation mode

Power flow from dc motor to dc supply.

Example

A half-wave controlled ^{and two phases a} rectifier with 110V phase voltage controls a dc motor with 9.9A. By assuming the load current continuous, For $\alpha = 60^\circ$,

- Draw circuit and find out the motor voltage
- Calculate the average current for each transistor
- Calculate the rms current
- Find out the active power drawn from network

Solution

a) $U_{d\alpha} = U_d \cdot \cos \alpha$

$$U_d = s \cdot \frac{q}{\pi} \cdot \sqrt{2} \cdot U_{\text{phase}} \cdot \sin \frac{\pi}{q}$$

$s = 1$ for half-wave

$q = 2$ two phase

$$U_{d\alpha} = 1 \cdot \frac{2}{\pi} \cdot \sqrt{2} \cdot 110 \cdot \sin \frac{\pi}{2} \cdot \cos 60^\circ$$

$$U_{d\alpha} = 49.52 \text{ V}$$

b) $I_{TAV} = \frac{1}{q} \cdot I_d \rightarrow \text{motor current} = \frac{1}{2} \cdot 9.9 \text{ A}$
 $= 4.95 \text{ A}$

c) $I_{T\text{rms}} = \sqrt{\frac{1}{q}} \cdot I_d = 7 \text{ A}$

d) $P_s \approx P_{\text{motor}} = 49.52 \cdot 9.9 = 490.2 \text{ W}$

